 


## 2. Timing.



Time relative to the beginning of a cycle.

a1. Reg-Ready. 1ns

a2. Control-Ready.  $1 + 2 = 3\text{ns}$

a3. Adder-Ready.  $1 + 10 = 11\text{ns}$

a4. Latest. The input to registers must be ready. This is the example in the figure.

The combinational circuit has their output ready 11 ns into a cycle. The setup time is 0.5 ns.

The minimum cycle time is:  $11 + 0.5 = 11.5\text{ ns}$ .

The highest clock rate is:  $1 / 11.5\text{ ns} = 0.08696\text{ GHz} = 87.0\text{ MHz}$

If we use the same kind of registers, the max clock rate we can achieve is  $1/(1\text{ns} + 0.5\text{ns}) = 0.6667\text{ GHz} = 666.7\text{ MHz}$ . In this case, there is no combinational circuit or no delay.

## 3. Multiplier.

$$27 * 17 = 459$$

0	0000011011	10001	0000000000
1	0000110110	01000	0000011011
2	0001101100	00100	0000011011
3	0011011000	00010	0000011011
4	0110110000	00001	0000011011
5	1101100000	00000	0111001011

If we consider the bits are two's complement number, 0b11011 is -5 and 0b10001 is -15. Their product is 75, which is 0b00010\_01011. The lowest five bits are the same as the lowest five bits in the product register.