

Homework 6

Benny Chen

November 7, 2022

Problem 1


Assume the single-cycle RISC-V processor, as shown in Figure 4.21. Find the following signal values when the processor executes the instruction 0xFE542023 located at 0x00400200. Explain your answers. All signals generated by the main control.

Instruction: 0x00400200 : 0xFE542023


Binary: 010000000000010000000000 : 1111111 00101 01000 010 00000 0100011

- opcode: $\text{instruction}[6:0] = 0100011 = 0x23$
- rs1: $\text{instruction}[19:15] = 01000 = 0x8$
- rs2: $\text{instruction}[24:20] = 00101 = 0x5$
- rd: $\text{instruction}[11:7] = 00000 = 0x0$
- Immediate: $\text{instruction}[11:5, 4:0] = 1111\ 1110\ 0000$ extended to 32 bits = 0xFFFFFFE0
- ALU operation: 0010
- BranchTarget: $0x00400200 + 0xFFFFFFE0 = 0x004001E0$
- PCSrc: 0
- NextPC: $0x00400200 + 4 = 0x00400204$

a.

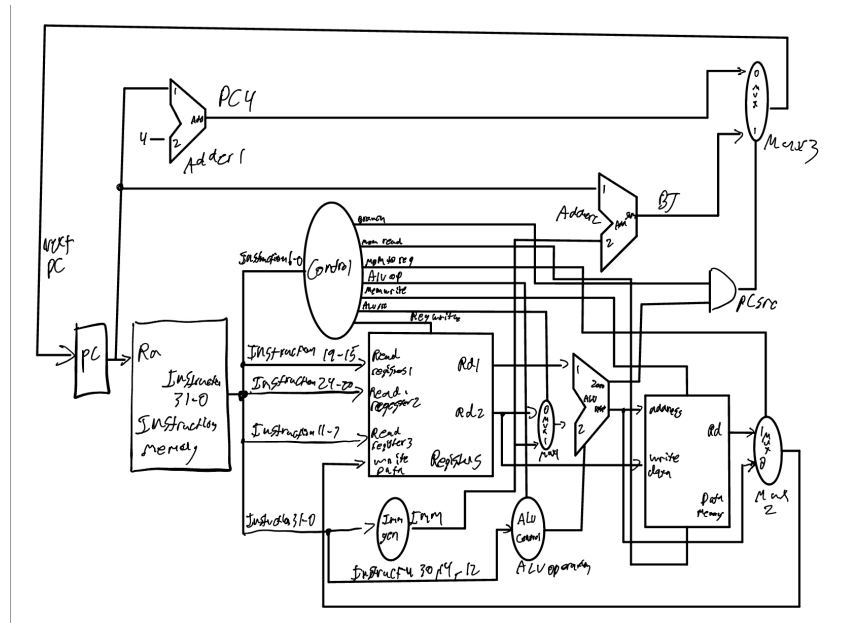

b.

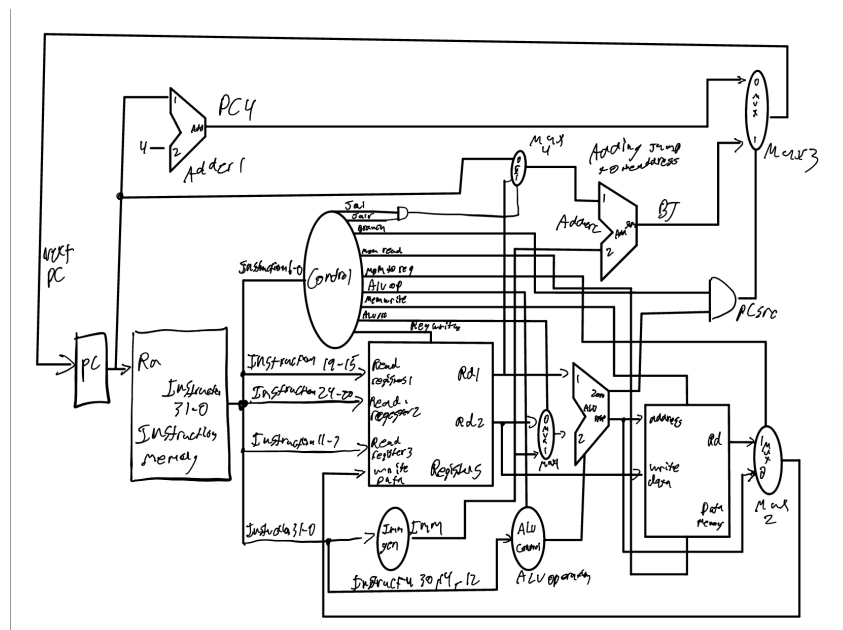

JAL: PC + Immediate JALR: RD (Read Data) + immediate c.

